

Feedback in Amplifiers

The term feedback implies transfer of energy from the output of a system to its input. The process of combining a fraction of the output energy (a, voltage or current) back to the input is called the feedback. The amplifiers which use the feedback principle, are known as feedback amplifiers.

A feedback amplifier mainly consists of two parts: an amplifier circuit and feed back circuit. Amplifier circuit amplifies the i/p signal and the function of feed back n/w is to return a fraction of o/p energy to the i/p of the amplifier. A feed back n/w may be consist of either passive elements like resistors, inductors or capacitors or active elements like transistors.


Classification of Feedback

Depending upon whether the feedback signal increases or decreases the input signal, the feedback may be classified into two types

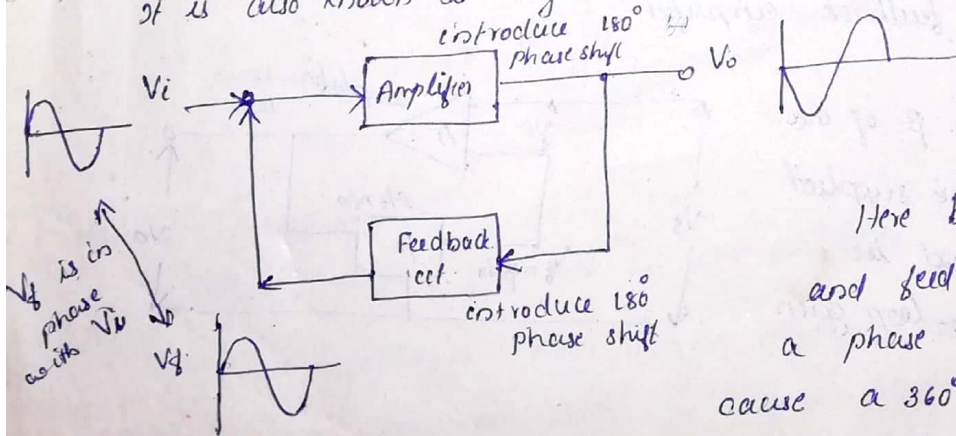- (1) Positive feedback
- (2) Negative feedback

Positive feedback

If the feedback signal applied is in phase with the i/p signal and thus increases it, then it is called a +ve feedback. It is also known as regenerative feedback or direct feedback.




Here both the amplifier and feedback n/w introduce a phase shift of 180° . This causes a 360° phase shift

around the loop and thus feedback signal is in phase with the input signal. +ve f/b causes excessive distortion and instability \therefore it is seldom used in amplifiers. Because of its

capability of increasing the power of the original signal, it is used in oscillator circuits.

Negative feedback

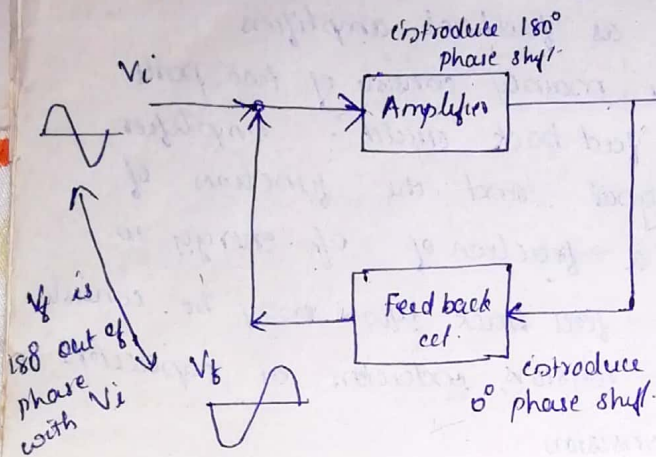If the feedback signal is ~~in~~ out of phase with the i/p signal and thus decreases it, then it is called -ve feed back. It is also known as degenerative feedback or inverse feedback.




Here amplifier introduces 180° and feedback n/c introduces 0° phase shift. Thus the feed back signal is ~~in~~ out of phase with the i/p signal.

-ve feedback reduces the amplifier gain but it has some advantages such as gain stability, reduction in non-linear distortion, reduction in noise, increase in bandwidth etc. \therefore -ve feedback is most widely used in amplifier circuit.

Principle of Feedback in Amplifiers

Consider an ordinary amplifier

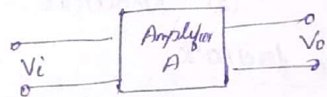
$$\text{Voltage gain, } A = \frac{\text{o/p voltage}}{\text{i/p voltage}} = \frac{V_o}{V_i}$$



$$A = \frac{V_o}{V_i} \rightarrow \text{open loop gain.}$$

Consider a feedback amplifier

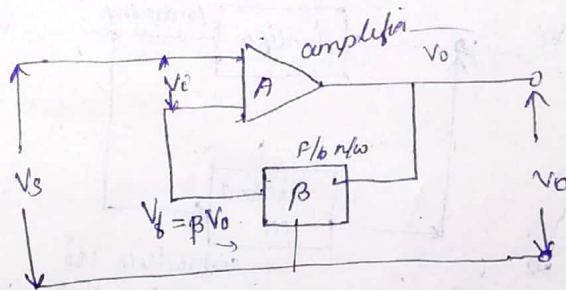Let a fraction β of the o/p voltage V_o be supplied back to i/p and let A be the open-loop gain



$$A = \frac{V_o}{V_i}$$

i/p voltage $V_i = V_s + V_f$

For +ve f/b $V_i = V_s + \beta V_o$

For -ve f/b $V_i = V_s - V_f = V_s - \beta V_o$

$$i.e. \quad V_i = V_s \pm \beta V_o$$

& we consider the $-ve$ feedback case

$$V_i = V_s - \beta V_o$$

here i/p voltage is equal to the i/p voltage $(V_s - \beta V_o)$ multiplied by the amplifier open loop gain A .

$$\therefore V_o = A (V_s - \beta V_o)$$

$$or \quad (1 + \beta A) V_o = A V_s$$

$$\frac{V_o}{V_s} = \frac{A}{1 + \beta A}$$

This is known as the voltage gain of the amplifier with feedback A_f . This is also known as the closed loop gain.

Hence voltage gain of with $-ve$ feedback will be

$$A_f = \frac{V_o}{V_s} = \frac{A}{1 + \beta A}$$

iii) voltage gain with $+ve$ feedback

$$A_f = \frac{A}{1 - \beta A}$$

$\beta A \rightarrow$ feedback factor

$A \rightarrow$ gain without feedback.

$(1 \pm \beta A) \rightarrow$ loop gain

$A_f \rightarrow$ gain with feedback.

$$A_f = \frac{A}{1 + \beta A}$$

a) if no feedback i.e. $\beta = 0$

$$then \quad A_f = A$$

$A + \beta \rightarrow$ phasor quantities having mag as well as phase.

b) if $1 + \beta A > 1$, then $-ve$ f/b

$$i.e. \quad A_f < A$$

c) if $1 + \beta A < 1$, then $+ve$ f/b

$$A_f > A$$

d) if $1 + \beta A = 0$

$$i.e. \quad A_f = \infty$$

it acts as an oscillator.

The feedback may also be classified as voltage feedback and current feedback. Both the voltage and current can be feedback to the i/p either in series or in $||^d$ which results in 4 basic feedback connections

Comparison of +ve f/b and -ve f/b

+ve feed back

Advantages:

gain of amplifier increases

disadvantages:

- gain is unstable
- produce distortion of the o/p signal.

-ve feedback

disadvantages

gain of amplifier decreases

advantages:

- * improves stability of gain
- * Reduction of non-linear distortion.
 - non linear distortion is reduced by a factor of $(1+AB)$.
- * Reduction of noise
 - reduced by a factor of $(1+AB)$
- * increase in bandwidth (improved frequency response)
- * increased in o/p impedance - \uparrow by a factor of $(1+AB)$
- * reduction in o/p impedance - \downarrow by a factor of $(1+AB)$

$(1-\beta A)$ is a complex quantity.

- 1) If $(1-\beta A)$ is less than unity, then A_f exceeds A . This condition corresponds to +ve f/b because voltage feedback adds to i/p signal voltage & yes V_{in} : +ve f/b, though \uparrow gain but it reduces the stability & yes the distortion & so avoided
- 2) If $(1-\beta A) = 0$, gain A_f becomes infinite. This is possible when e/p is zero. Then the amp is then capable of giving o/p voltage even with zero signal operation as an amplifier.
- 3) If $(1-\beta A) > \text{unity}$ then $A_f < A$. This means f/b voltage V_{in} becomes smaller than V_{in} . This corresponds to -ve f/b. Though -ve f/b reduces the gain of the amp but improves its performance.

Q) A single stage tr. amp has a voltage gain of 600 without f/b & 50 with f/b. Calcul: % of o/p which is fed back to i/p

$$A = 600, A_f = 50$$

$$A_f = \frac{A}{1+AB} \Rightarrow \text{or } \beta = 0.01833$$

$$\frac{V_p}{V_i} \times 100 = \beta \times 100 = 0.01833 \times 100 = 1.833\%$$