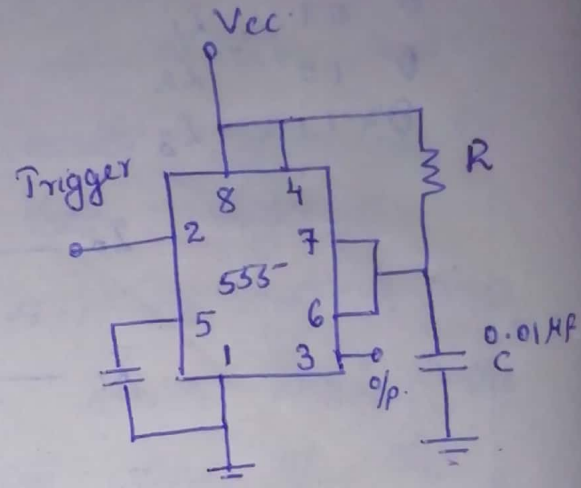


Q. 2

Q. In the monostable multivibrator ckt, $R = 100 \text{ k}\Omega$ and the time delay $T = 100 \text{ ms}$. Calculate the value of C .




Ans.

$$T = 1.1RC$$

$$C = \frac{T}{1.1R} = \frac{100 \times 10^{-3}}{1.1 \times 100 \times 10^3} = \underline{\underline{0.9 \mu\text{F}}}$$

Q. In the astable multivibrator ckt, $R_A = 6.8 \text{ k}\Omega$, $R_B = 3.3 \text{ k}\Omega$ and $C = 0.1 \mu\text{F}$. Calculate

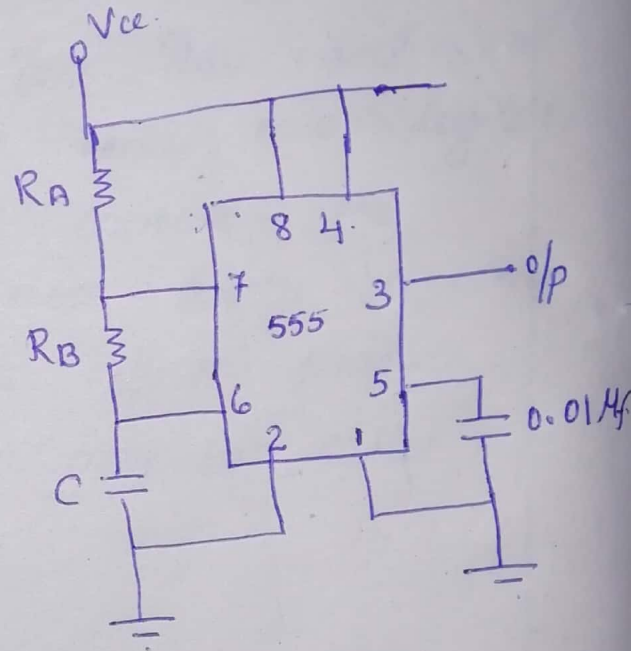- (a) T_{high} (b) T_{low} (c) free running frequency (d) duty cycle.



Ans.

$$\begin{aligned} \text{(a)} \quad T_{\text{high}} &= 0.69(R_A + R_B)C \\ &= 0.69(6.8 \times 10^3 + 3.3 \times 10^3)0.1 \mu\text{F} \\ &= \underline{\underline{0.7 \text{ ms}}} \end{aligned}$$

$$\begin{aligned} \text{(b)} \quad T_{\text{low}} &= 0.69R_B C = 0.69 \times 3.3 \times 10^3 \times 0.1 \times 10^{-6} \\ &= \underline{\underline{0.23 \text{ ms}}} \end{aligned}$$

$$\textcircled{c} \quad f = \frac{1}{T} = \frac{1}{T_{\text{high}} + T_{\text{low}}} = \frac{1}{0.7 + 0.23}$$

$$= \underline{\underline{1.07 \text{ kHz}}}$$

or

$$f = \frac{1.45}{(R_A + 2R_B)C} = \frac{1.45}{(6.8 \times 10^3 + 2 \times 3.3 \text{ k}\Omega) 0.1 \mu\text{F}}$$

$$= \underline{\underline{1.07 \text{ kHz}}}$$

$$\textcircled{d} \quad \text{Duty cycle} = \frac{T_{\text{high}}}{T} \times 100 = \frac{0.7 \text{ ms}}{\cancel{0.7} + 0.23} \times 100$$

$$= \underline{\underline{75 \%}}$$

Frequency of oscillations,

$$f = \frac{1}{T} = \frac{1}{1.4 \text{ ms}} = 714.3 \text{ Hz Ans.}$$

$$\text{Duty cycle} = \frac{T_{\text{HIGH}}}{T} = \frac{0.707}{1.4} = 50.5\% \text{ Ans.}$$

Example 33.2. Determine the positive pulse width, negative pulse width and free running frequency for an astable multivibrator using 555 timer. $R_A = 4.7 \text{ k}$, $R_B = 1 \text{ k}$, $C = 1 \mu\text{F}$, $C_1 = 0.01 \mu\text{F}$. What is the duty cycle of output waveform?

Solution :

$$T_{\text{on}} = 0.693 (R_A + R_B) C$$

$$= 0.693 (4.7 + 1) 10^3 \times 1 \times 10^{-6}$$

$$= 3.95 \text{ ms Ans.}$$

$$T_{\text{off}} = 0.693 R_B C = 0.693 \times 1 \times 10^3 \times 1 \times 10^{-6}$$

$$= 0.693 \text{ ms Ans.}$$

$$f = \frac{1.4}{(R_A + 2R_B)C}$$

$$= \frac{1.4}{(4.7 + 2 \times 1) 10^3 \times 1 \times 10^{-6}} = 208.9 \text{ Hz Ans.}$$

$$D = \frac{R_A + R_B}{R_A + 2R_B} \times 100 = \frac{4.7 + 1}{4.7 + 2 \times 1} \times 100$$

$$= 85\% \text{ Ans.}$$

Example 33.3. The timer IC555 is used as astable multivibrator. It is desired to have square-wave output with 50% duty cycle of 1 kHz. The timing capacitor is of $0.01 \mu\text{F}$. Find the values of resistors required and draw the circuit.

Solution : For 50% duty cycle

$$T_{\text{on}} = T_{\text{off}} = \frac{T}{2}$$

$$R_A = R_B$$

$$C = 0.01 \mu\text{F} = 1 \times 10^{-8} \text{ F}$$

$$f = 1 \text{ kHz} = 1,000 \text{ Hz}$$

Frequency is given by equation


$$f = \frac{1.44}{(R_A + R_B)C} = \frac{1.44}{2R_A C}$$

$$\text{or } R_B = R_A = \frac{1.44}{2 \times f \times C}$$

$$= \frac{1.44}{2 \times 1,000 \times 1 \times 10^{-8}}$$

$$= 72 \text{ k}\Omega \text{ (68 k}\Omega \text{ standard value) Ans.}$$

Circuit diagram is shown in Fig. 33.12.

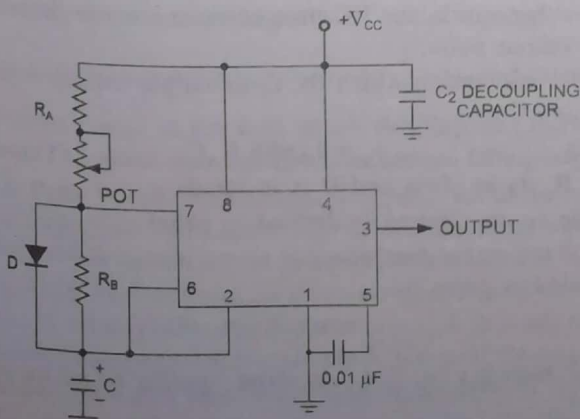

Example 33.4. Design a 555 timer as an astable multivibrator with an output signal frequency of 800 Hz and 60 percent duty cycle. [U.P. Technical Univ. Analog Integrated Circuits 2005-06]

Solution : Percent duty cycle,

$$D = \frac{R_A + R_B}{R_A + 2R_B} \times 100 = 60 \text{ [Refer to Eq. (33.5)]}$$

$$\text{or } R_A + R_B = 0.6R_A + 1.2R_B$$

$$\text{or } R_B = 2R_A$$

Frequency is given by

$$f = \frac{1.44}{(R_A + 2R_B)C} \quad \dots [\text{Refer to Eq. (33.4)}]$$

Substituting $f = 800 \text{ Hz}$, $R_B = 2R_A$ and $C = 0.01 \mu\text{F}$ (assumed value in above equation) we have

$$800 = \frac{1.44}{5R_A \times 0.01 \times 10^{-6}}$$

$$\text{or } R_A = \frac{1.44}{800 \times 5 \times 0.01 \times 10^{-6}} = 36,000 \Omega \text{ or } 36 \text{ k}\Omega$$

$$\text{and } R_B = 2R_A = 2 \times 36 = 72 \text{ k}\Omega$$

$$\text{Thus } C = 0.01 \mu\text{F}; R_A = 36 \text{ k}\Omega \text{ and } R_B = 72 \text{ k}\Omega \text{ Ans.}$$

Example 33.5. Design a 555 timer as an astable multivibrator with an output signal frequency of 700 Hz and 50% duty cycle. [U.P. Technical Univ. Analog Integrated Circuits 2004-05]

Solution : For 50% duty cycle

$$T_{\text{on}} = T_{\text{off}}$$

$$R_A = R_B$$

and frequency is given by equation

$$f = \frac{1.44}{(R_A + R_B)C}$$

Substituting $f = 700 \text{ Hz}$; $R_B = R_A$ and $C = 0.01 \mu\text{F}$ (assumed value) in above equation, we have

$$700 = \frac{1.44}{2R_A \times 0.01 \times 10^{-6}}$$

$$\text{or } R_A = R_B = \frac{1.44}{700 \times 2 \times 0.01 \times 10^{-6}}$$

$$= 103 \text{ k}\Omega \text{ (100 k}\Omega \text{ standard value)}$$

$$\text{Thus } C = 0.01 \mu\text{F}$$

$$R_A = R_B = 100 \text{ k}\Omega \text{ Ans.}$$

Example 33.6. Determine the frequency of the free-running ramp generator circuit given in Fig. 33.7 (a) if $C = 0.05 \mu\text{F}$, $R = 12 \text{ k}\Omega$, $V_{CC} = 5 \text{ V}$ and $V_{BE} = V_{D1} = 0.7 \text{ V}$.

Solution : Collector current,

$$I_C = \frac{V_{CC} - V_{BE}}{R} = \frac{5 - 0.7}{12 \times 10^3} = 0.000358 \text{ A}$$

Free-running frequency,

$$f_0 = \frac{3I_C}{V_{CC} \times C} = \frac{3 \times 0.000358}{5 \times 0.05 \times 10^{-6}} = 4.3 \text{ kHz Ans.}$$

33.7. THE 555 TIMER AS A MONOSTABLE MULTIVIBRATOR

A monostable multivibrator (MMV) often called a *one-shot multivibrator* is a pulse generator circuit in which the