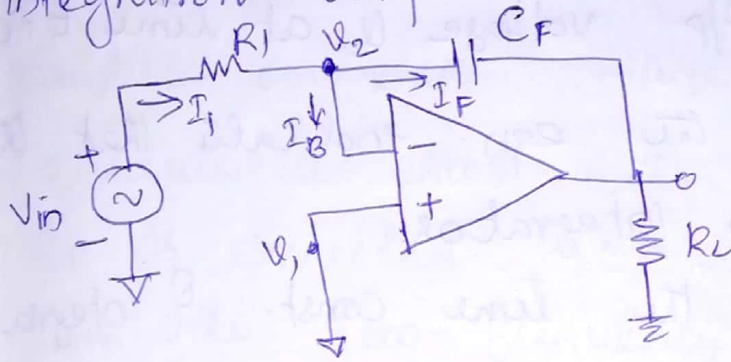


OpA Integrator

A ckt in which the op voltage is integral of ip voltage is the integrator or the integration amplifier



In the inv amp the R_f is replaced with a capacitor C_f .

Write KCL at node V_2

$$I_1 = I_B + I_F$$

Since I_B is negligibly small

$$I_1 \cong I_F$$

OpA capacitor current $I_C = C \frac{dV_C}{dt}$

$$\therefore \frac{V_{in} - V_2}{R_1} = C_F \frac{d}{dt} (V_2 - V_o)$$

How ever $V_1 = V_2 = 0$ (virtual gnd)

$$\frac{V_{in}}{R_1} = C_F \frac{d}{dt} (-V_o)$$

Integrating both sides w.r. to time




$$\begin{aligned} \int_0^t \frac{V_{in}}{R_1} dt &= \int_0^t C_F \frac{d}{dt} (-V_o) \\ &= C_F V_o + V_o|_{t=0} \end{aligned}$$

$$V_o = -\frac{1}{R_1 C_F} \int_0^t V_{in} \cdot dt + C$$

$C \rightarrow$ integration const and is proportional to the value of the o/p voltage V_o at time $t=0$ sec

-ve sign in the eqn. indicates that the circuit is an inverting integrator.

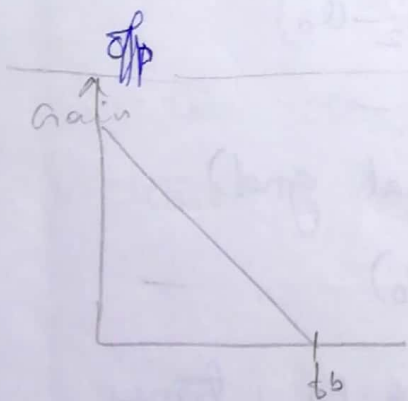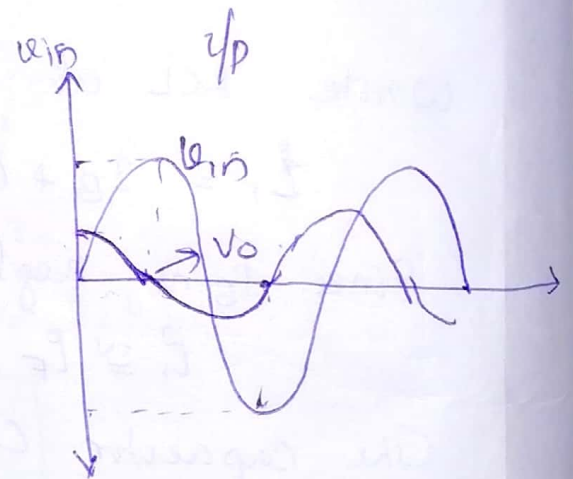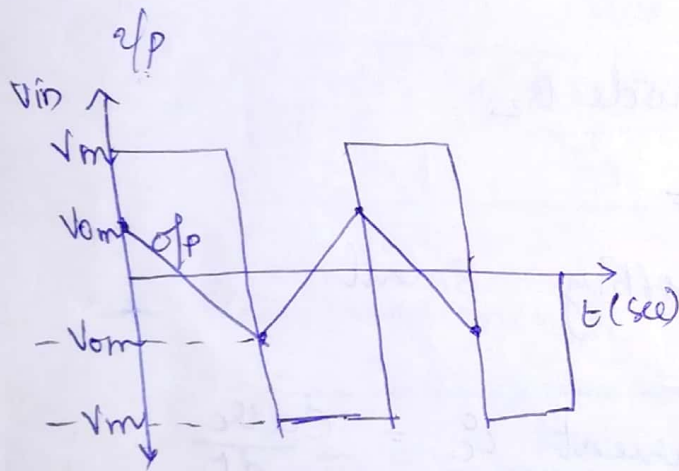$R_1 C_F$ is the time const. of integrator.



o/p

$$f_b = 10 f_a$$

Generally $f_a < f_b$. If $f_a = f_b/10$ then $R_F = 10 R_i$.
The op signal will be integrated properly if the time period T of the signal is larger than or equal to $R_F C_F$.

$$T \geq R_F C_F$$

$$\text{When } R_F C_F = \frac{1}{2\pi f_a}$$

if $f_{in} < f_a \rightarrow$ No integration

$f_{in} = f_a \rightarrow 50\%$ integration

$f_{in} = 10 f_a \rightarrow 99\%$ of accuracy

The integrator is most commonly used in analog computers and, ADC and signal wave shaping circuits.

The Differentiator


Differentiator or differentiation amplifier performs mathematical operation of differentiation. i.e., op waveform is the derivative of ip waveform.

By KCL

$$I_C = I_B + I_F$$

Since $I_B = 0$

$$I_C = I_F$$

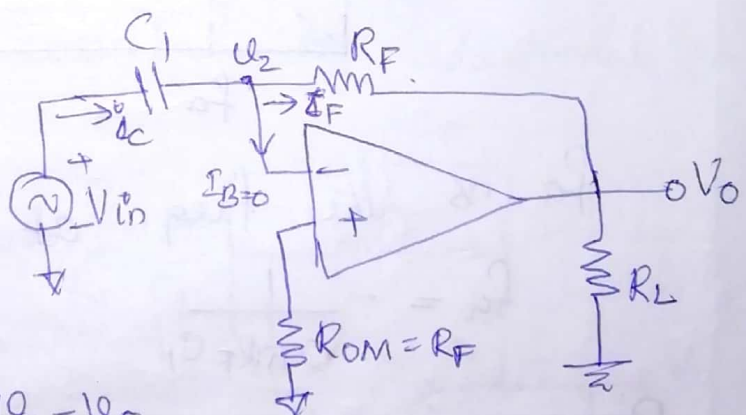

$$C_1 \frac{d(V_{in} - V_2)}{dt} = \frac{V_2 - V_o}{R_F}$$


But $V_2 = 0$ (virtual ground)

$$C_1 \frac{dV_{in}}{dt} = - \frac{V_o}{R_F}$$

$$\therefore V_o = -R_F C_1 \frac{dV_{in}}{dt}$$

The gain of the circuit $\left(\frac{R_F}{X_{C1}}\right)$ increases in freq. at a rate of 20dB/dec. This makes the ckt unstable. X_{C1} decreases with ^{increase in} freq. which makes the ckt very susceptible to high freq. noise.

Freq. response of differentiator

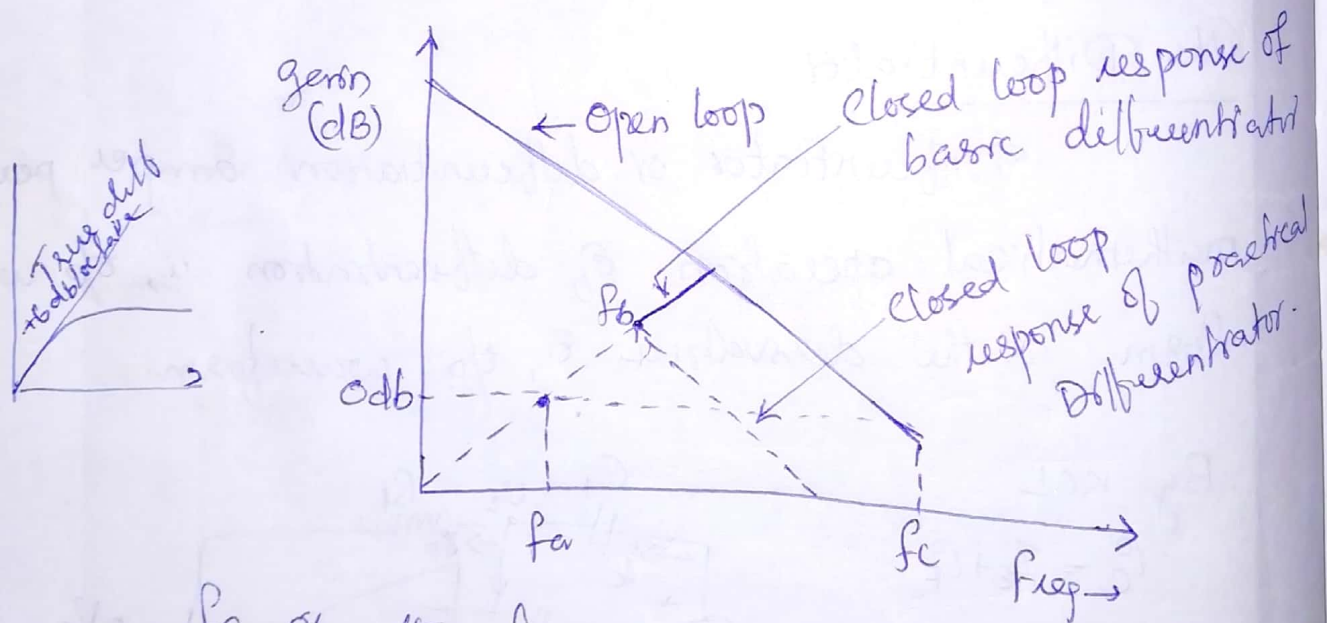

f_a is the freq. at which gain is 0dB.

$$f_a = \frac{1}{2\pi R_F C_1}$$

Proof.

$$\frac{V_o(s)}{V_{in}(s)} = \frac{-Z_F(s)}{Z_i(s)}$$

where $Z_F(s) = R_F$ and $Z_i(s) = \frac{1}{sC_1}$