
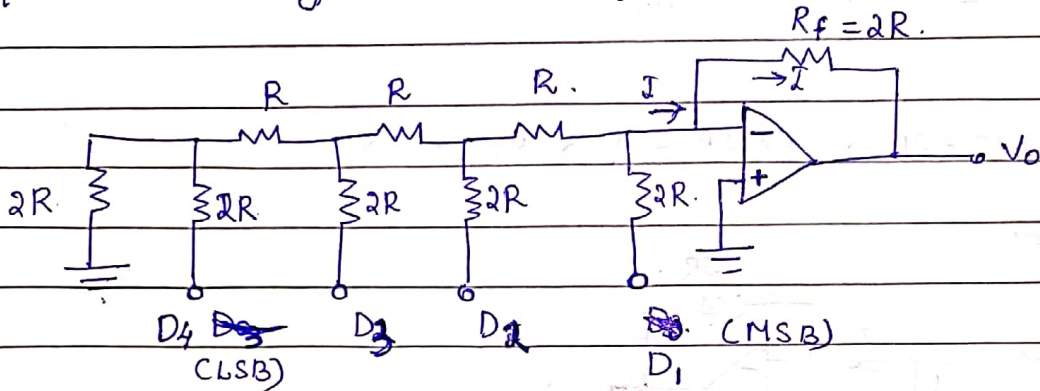


R-2R DAC

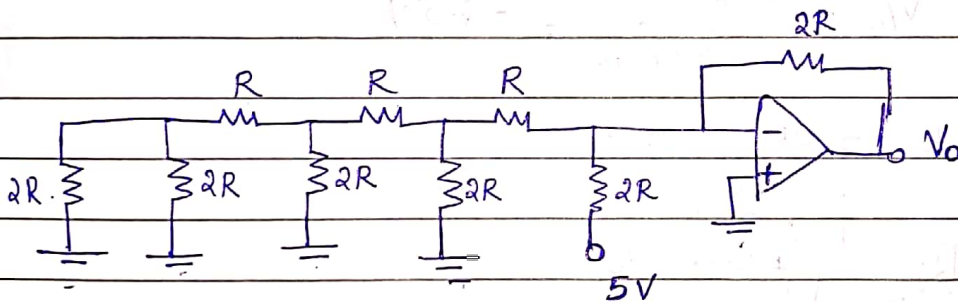
Wide range of resistors used in binary weighted type DAC. It can be avoided by using R-2R ladder type DAC where only two values of resistors are required. The typical value of R ranges from $2.5\text{ k}\Omega$ to $10\text{ k}\Omega$.



Consider a 4-bit DAC where the switch position $D_1 D_2 D_3 D_4$ corresponds to the binary word 1000. i.e. $D_1 = 1$ and other i/p's = 0.


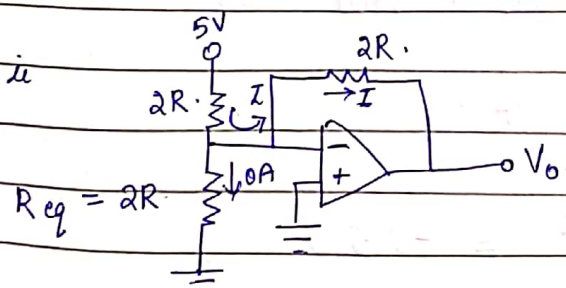
$$\mu \quad \frac{2R \times 2R}{2R + 2R} = R \rightarrow R + R = 2R \rightarrow \frac{2R \times 2R}{2R + 2R} = R \rightarrow R + R = 2R \rightarrow \frac{2R \times 2R}{2R + 2R} = R \rightarrow R + R = 2R$$




$$\mu \quad R_{eq} = \left(\left\{ \left[(2R \parallel 2R) + R \right] \parallel 2R \right\} + R \right) \parallel 2R$$

$+ R = 2R$


There is essentially no current through $2R$ equivalent resistance. Thus all the current $I = \frac{5V}{2R}$ goes through R_f .

$$\therefore V_o = -I R_f = -\frac{5V \times 2R}{2R} = -5V$$

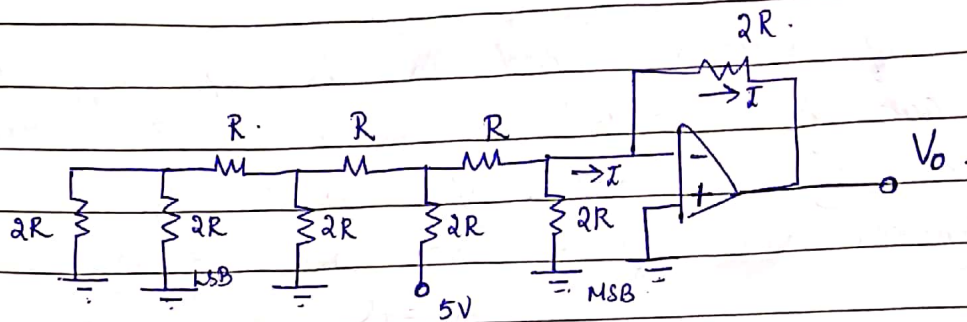★ Consider the input 0100. . . ie $D_2 = 1$ & all others = 0



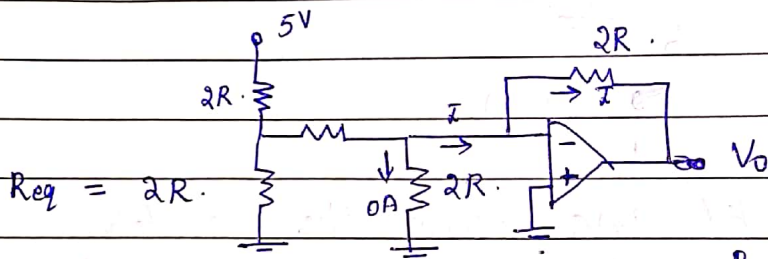
$$\frac{2R \times 2R}{2R + 2R} = R \rightarrow R + R = 2R \rightarrow \frac{2R \times 2R}{2R + 2R} = R \rightarrow R + R = 2R$$



$$R_{eq} = \left\{ \left(\frac{2R \parallel 2R}{2R} \right) + R \right\} \parallel 2R = 2R$$

$$V_H = \frac{-5 \times 2R}{2R + 2R} = -2.5V$$


$$R_H = 2R \parallel 2R = R$$

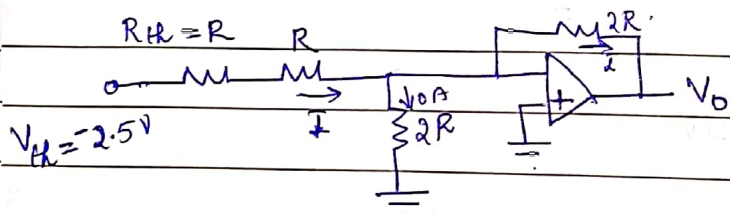


No current flows through $2R$. Thus all current $I = \frac{2.5}{2R}$ goes through R_f .

$$\therefore V_o = -I R_f = \frac{-2.5}{2R} \times 2R = -2.5V$$

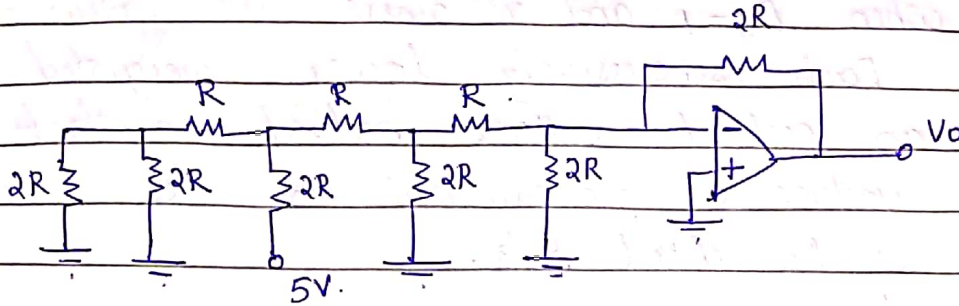★ Consider the input 0010. i.e. $D_3 = 1$ and all other grounded.



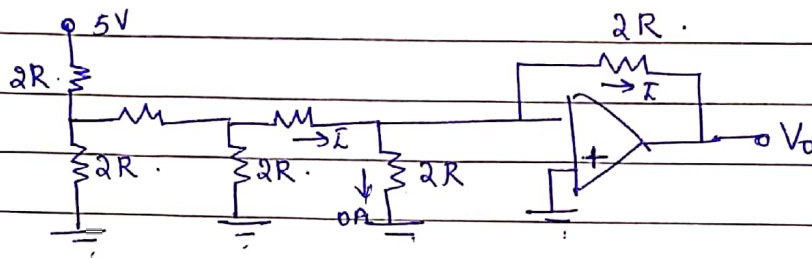
$$\frac{2R \times 2R}{2R + 2R} = R \rightarrow R + R = 2R.$$




$$V_{th1} = \frac{-5 \times 2R}{2R + 2R} = -2.5V.$$

$$R_{th1} = 2R \parallel 2R = R.$$

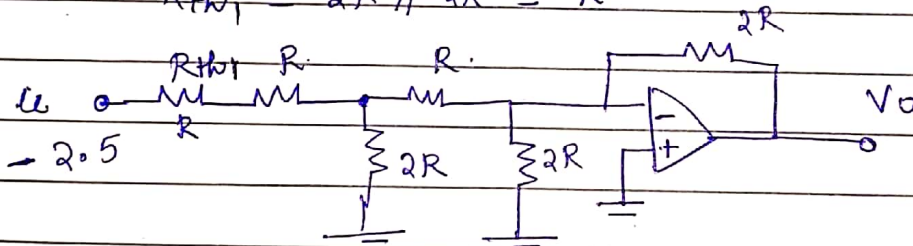

Again $V_{th2} = \frac{-2.5 \times 2R}{2R + 2R} = -1.25$

$$R_{th2} = 2R \parallel 2R = R.$$

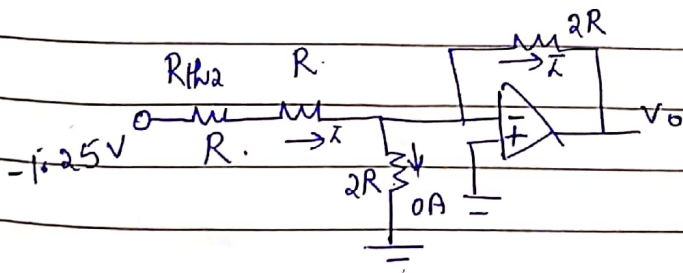

No current flows through $2R$.

Thus all current $I = \frac{-1.25}{2R}$ goes through R_f .

$$V_o = \frac{-1.25 \times 2R}{2R} = -1.25V$$

Similarly when $D_4 = 1$ and all others are grounded.
 $V_o = -0.625V$. Each successively lower weighted
i/p produces an output voltage halved, so that
the output voltage is proportional to the
binary weight of the input bits.