


## Instrumentation Amplifier

The physical quantities (eg. temp., humidity, light intensity etc) are usually measured with the help of transducers. The o/p of transducers amplified so that it can drive the indicators or display system. This function is performed by an instrumentation amplifier.

The important features of an instrumentation amplifier

- (1) High gain accuracy
- (2) High CMRR.
- (3) High gain stability with low temp. coefficient
- (4) Low dc offset
- (5) Low o/p impedance
- (6) High i/p resistance.
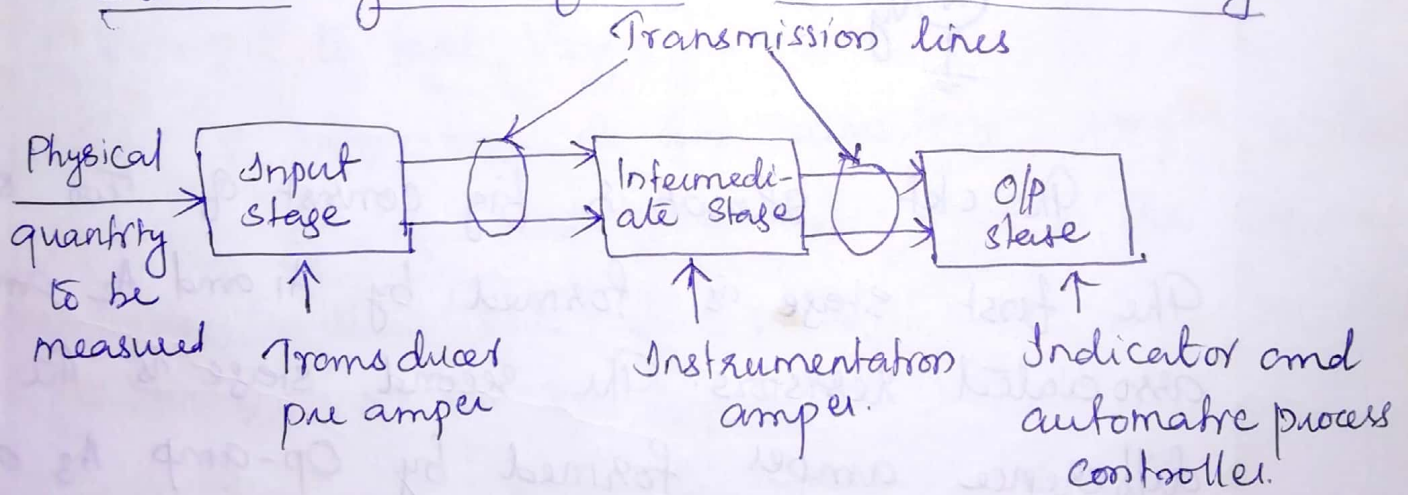
### Block diagram of an instrumentation system.




An instrumentation system is used to measure the o/p signal produced by a transducer and often to control the physical signal producing it.

The i/p stage composed of a pre-amplifier and some sort of transducer. The o/p stage may

use the devices such as meters, oscilloscopes, charts etc.

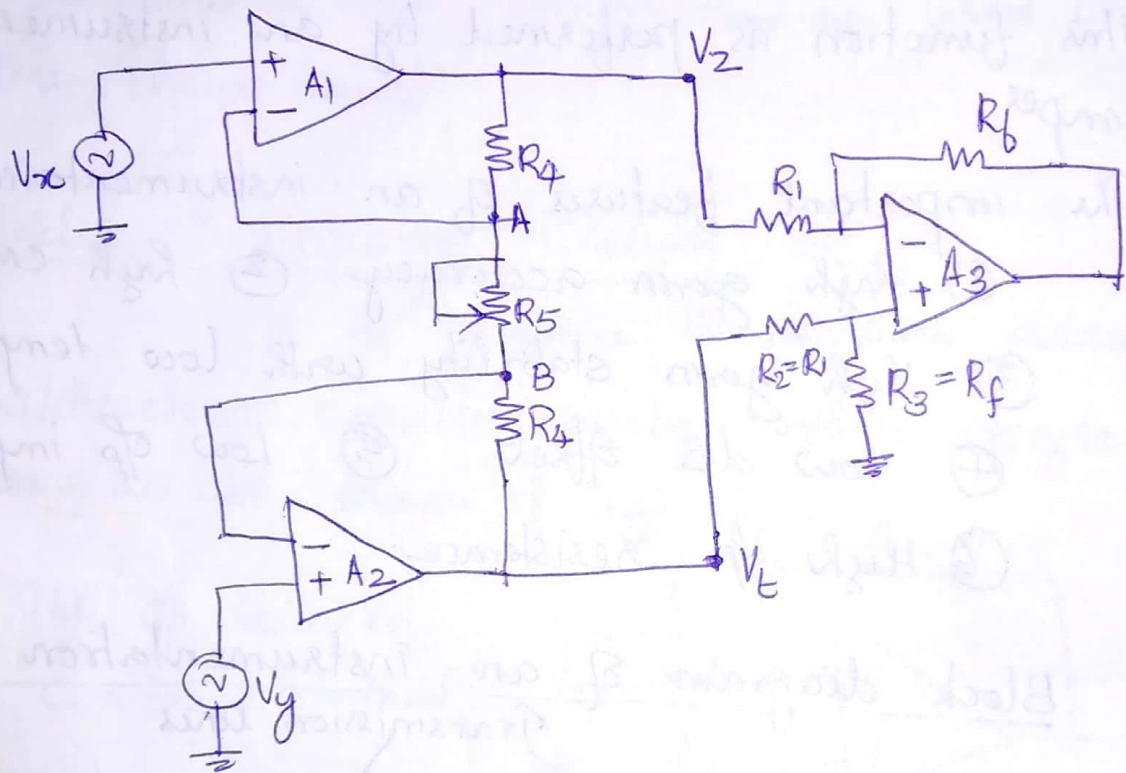Instrumentation Amplifier (Differential amplifier with three op-amp)



The ckt shown is in fact consists of two stages. The first stage is formed by  $A_1$  and  $A_2$  and their associated resistors. The second stage is the difference amplifier formed by Op-amp  $A_3$  and its four associated resistors.

The op of instrumentation amplifier or the op of differential amplifier is

$$V_o = -\frac{R_f}{R_1} (V_z - V_L) \quad \text{--- (1)}$$



where  $V_z$  and  $V_t$  are the op voltages to the difference amp. Also  $V_z$  is the o/p of op-amp  $A_1$  and  $V_t$  is the o/p of op-amp  $A_2$ .

$V_z$  can be obtained using superposition theorem

$$V_z = V_{zx} + V_{zy}$$

$V_{zx} \rightarrow V_z$  due to  $V_x$  alone

$V_{zy} \rightarrow V_z$  due to  $V_y$  alone

Case 1

$V_y = 0$  to find  $V_{zx}$ .

When  $V_y = 0$  node B is at virtual gnd or  $V_B = 0V$ .

Thus  $A_1$  is now a non-inv amp with  $R_f = R_4$  and  $R_i = R_5$

$$\therefore V_{zx} = \left(1 + \frac{R_4}{R_5}\right) V_x.$$

Case 2

$V_x = 0$  to find  $V_{zy}$ .

When  $V_x = 0V$ ,  $A_1$  is an inverting amp with

$R_f = R_4$ ,  $R_i = R_5$  and  $V_i = V_B$ . Since the op-amp terminals will track the potential  $V_B = V_y$

(since  $V_{id} = 0$  in op-amp  $A_2$ )

$$V_y - V_B = 0V \text{ or } V_B = V_y.$$

$$\text{Thus } V_{zy} = -\frac{R_4}{R_5} V_B = -\frac{R_4}{R_5} V_y.$$

Hence the net o/p of op-amp  $A_1$  is

$$V_z = V_{zx} + V_{zy} = \left(1 + \frac{R_4}{R_5}\right) V_x - \frac{R_4}{R_5} V_y \quad \text{--- (2)}$$

Since the circuit of instrumentation amplifier is symmetric the net o/p of op-amp A2 can be obtained in the similar manner as

$$V_t = V_{tx} + V_{ty} = \left(1 + \frac{R_4}{R_5}\right) V_y - \frac{R_4}{R_5} V_x \quad \text{--- (3)}$$

The o/p of instrumentation amplifier can now be obtained by substituting (2) and (3) in (1).

$$\therefore V_o = -\frac{R_f}{R_1} (V_2 - V_t)$$

$$= -\frac{R_f}{R_1} \left[ \left(1 + \frac{R_4}{R_5}\right) V_x - \frac{R_4}{R_5} V_y \right] - \left[ \left(1 + \frac{R_4}{R_5}\right) V_y - \frac{R_4}{R_5} V_x \right]$$

$$= -\frac{R_f}{R_1} \left[ \left(1 + \frac{R_4}{R_5}\right) (V_x - V_y) + \frac{R_4}{R_5} [V_x - V_y] \right]$$

$$= -\frac{R_f}{R_1} \left[ \left(1 + \frac{R_4}{R_5} + \frac{R_4}{R_5}\right) (V_x - V_y) \right]$$

$$\boxed{V_o = -\frac{R_f}{R_1} \left(1 + \frac{2R_4}{R_5}\right) (V_x - V_y)}$$

The difference mode gain of instrumentation

amplifier is  $\boxed{A_D = \frac{V_o}{V_x - V_y} = -\frac{R_f}{R_1} \left(1 + \frac{2R_4}{R_5}\right)}$

The common mode gain will be zero because of the differencing action of the second



stage ampers. Since both the sources  $V_x$  and  $V_y$  are connected to non inv. configurations, the i/p resistance seen by both the sources will be same. The i/p resistance seen by both the sources will be

$$R_{in} = R_{iy} = R_o(1 + A\beta) \quad \text{where } \beta = \frac{R_4 + R_5}{2R_4 + R_5}$$

$R_o \rightarrow$  i/p impedance resistance of op-amp and  
 $A' \rightarrow$  op-amp open loop gain.

The input impedance is very large ideally infinite is an advantage.

The difference gain of the amp can be varied by varying pot  $R_5$ .

This ckt also has high differential gain. Also if  $A_1$  and  $A_2$  and its corresponding resistors are matched, the signal paths are symmetric. is an adv. of the design of differential amp.

V to T and T to V connections