

Expression for Capacitor Voltage

$$V_c = V_f + (V_i - V_f) e^{-t/RC}$$

$$V_i = \frac{1}{3} V_{cc} \quad \& \quad V_f = V_{cc}$$

$$V_c = V_{cc} + \left[\frac{1}{3} V_{cc} - V_{cc} \right] e^{-t/RC}$$

At time $t = T_{HIGH}$ $V_c = \frac{2}{3} V_{cc}$

$$\frac{2}{3} V_{cc} = V_{cc} + \left[\frac{1}{3} V_{cc} - V_{cc} \right] e^{-T_{HIGH}/RC}$$

$$\frac{2}{3} = 1 + \left(\frac{1}{3} - 1 \right) e^{-T_{HIGH}/RC}$$

$$\frac{2}{3} e^{-T_{HIGH}/RC} = \frac{1}{3}$$

$$T_{HIGH} = 0.69 RC$$

Capacitor charges through R_A & R_B $\therefore T_{HIGH} = 0.69 (R_A + R_B) C$

The o/p is low while the capacitor discharges from $\frac{2}{3} V_{cc}$ to $\frac{1}{3} V_{cc}$

Voltage across capacitor $V_c = V_f + (V_i - V_f) e^{-t/RC}$

$$V_f = 0 \quad \& \quad V_i = \frac{2}{3} V_{cc} \Rightarrow V_c = 0 + \left(\frac{2}{3} V_{cc} - 0 \right) e^{-t/RC}$$

At $t = T_{LOW}$ $V_c = \frac{1}{3} V_{cc}$

$$\frac{1}{3} V_{cc} = \frac{2}{3} V_{cc} e^{-T_{LOW}/RC}$$

$$T_{LOW} = 0.69 R_B C$$

Capacitor discharges through R_B $\therefore T_{LOW} = 0.69 R_B C$

$$\text{Total Time} = T_{HIGH} + T_{LOW}$$

$$T = 0.69 (R_A + 2R_B) C$$


$$f = \frac{1}{T} = \frac{1.45}{(R_A + 2R_B) C}$$

$$\% \text{ Duty cycle} = \frac{T_{HIGH}}{T} \times 100 = \frac{0.69 (R_A + R_B) C}{0.69 (R_A + R_B) C + 0.69 R_B C}$$

To get 50% Duty cycle R_A must be reduced to zero. It is not practically possible because high current will flow through Q_1 & damage Q_1 .

An alternative circuit to set duty cycle 50% is shown in Fig.

 During charging D_1 is forward biased effectively short circuiting R_B so that $T_{HIGH} = 0.69 R_A C$



During discharging portion Q_1 ON and grounding pin 7, hence D_1 is in reverse biased condition. So $T_{Low} = 0.69 R_B C$

$$T = T_{High} + T_{Low} = 0.69 (R_A + R_B) C$$

$$f = \frac{1}{T} = \frac{1.45}{(R_A + R_B) C}$$

$$\text{Duty cycle} = \frac{R_B}{R_A + R_B} \quad \text{If } R_A = R_B \quad \% \text{ Duty cycle} = 50\%$$

PHASE LOCKED LOOP (PLL)

A Phase Locked loop (PLL) is basically a closed loop feedback system. The action of the PLL is to lock the o/p frequency and phase to the frequency and phase of i/p signal.

Operating Principles of PLL

The PLL is a circuit which causes a particular system to track with another one i.e. PLL synchronizes an o/p with an i/p signal in frequency as well as phase. In synchronized state or locked state the phase error between the oscillator's o/p and the i/p signal is zero or very small.

If the phase error builds up, a control mechanism acts on the oscillator in such a way that the phase error is again reduced to a minimum i.e. phase of o/p signal is actually locked to the phase of the i/p signal. That is why it is referred to as phase locked loop.

Block Diagram