

- Q) Design an inverting amplifier with gain $\bullet 10$ and ~~its~~ input resistance equal to $10\text{ k}\Omega$.

For an inverting amplifier,

$$\text{gain} = -\frac{R_f}{R_i}$$

$$\begin{aligned}\therefore R_f &= \text{gain} \times R_i \\ &= 10 \times 10\text{ k}\Omega \\ &= \underline{\underline{100\text{ k}\Omega}}\end{aligned}$$

- Q) ~~Design~~ Design a non inverting amplifier with gain 9.

For non inverting amp,

$$\text{gain} = 1 + \frac{R_f}{R_i}$$

$$\therefore 1 + \frac{R_f}{R_i} = 9$$

$$\frac{R_f}{R_i} = 9 - 1 = 8$$

$$\text{Let } R_i = 10\text{ k}\Omega$$

$$\therefore R_f = 10\text{ k} \times 8 = \underline{\underline{80\text{ k}\Omega}}$$