

Since C is unclamped, the Voltage across it rises exponentially through R towards V_{CC} with a time const RC . After a time period T the Capacitor Voltage is just greater than $\frac{2}{3}V_{CC}$ and the UC resets the FF. This makes $\bar{Q}=1$, Q , turns on thereby discharging the Capacitor C rapidly to gnd potential. The o/p is Zero i.e returns to a Stand by state.

The Voltage across the Capacitor $V_c = V_f + (V_i - V_f)e^{-t/RC}$

$$V_i = V_{cc} = 5 \quad V_i = 0 \quad \therefore V_c = V_{cc} [1 - e^{-t/RC}]$$

at $t = T$, $V_c = \frac{2}{3} V_{cc}$


$$2/3 V_{cc} = V_{cc} [1 - e^{-T/Rc}]$$

$$\frac{2}{3} = 1 - e^{-T/RC} \Rightarrow e^{-T/RC} = \frac{1}{3}$$

$$-T/R_C = \ln 1/3 = -1.098$$

$$T = 1.1RC \text{ Seconds}$$

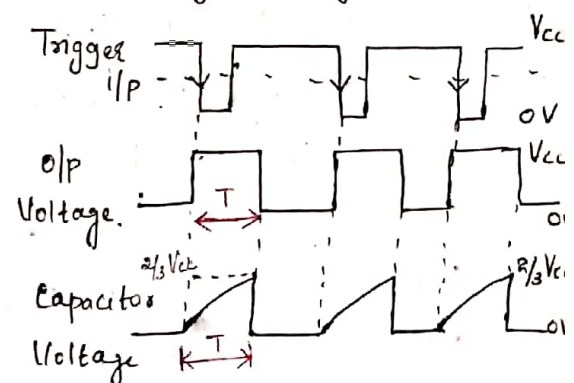
The timing interval is independent of the supply voltage. Once triggered, o/p remains high until the time T elapses, which depends on R and C . Any additional trigger coming during this time will not change the o/p state. But if a reset signal is applied the 555 circuit will be in reset condition and o/p is Zero.



ASTABLE MULTIVIBRATOR USING IC 555

An astable Multivibrator often called a free running multivibrator. It does not require an external trigger to change the state of the o/p, hence the name free running.

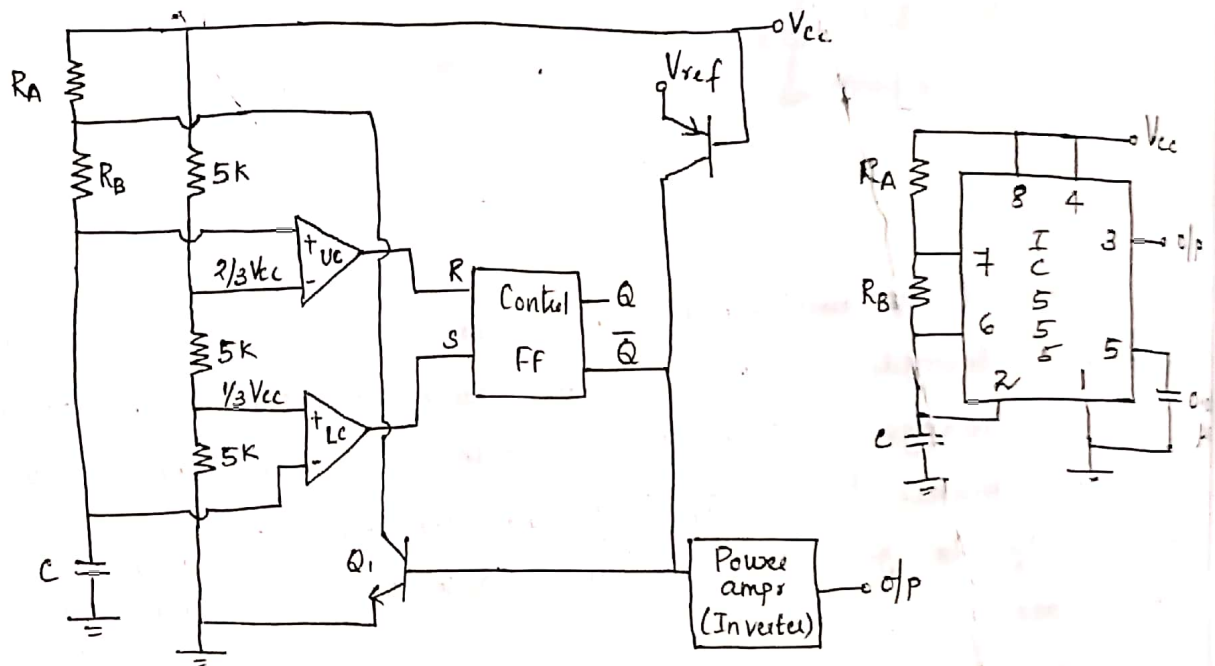The time during which the o/p is either high or low is determined by two resistors and a Capacitor which are externally connected to the 555 timer.



Working:

When the power supply V_{cc} is connected the external timing capacitor C charges toward V_{cc} with time Const $(R_A + R_B)C$. During this time the o/p is equal to HIGH (i.e. initially the capacitor voltage is zero and o/p of U_C is LOW and o/p of L_C is HIGH i.e. $R=0$ and $S=1$, FF sets i.e. $\bar{Q}=0$ and o/p = 1).

When the capacitor voltage is just greater than $\frac{2}{3}V_{cc}$ the U_C triggers and $R=1$ which resets the FF and $\bar{Q}=1$. Hence o/p is zero. This in turn makes Q_1 ON and the capacitor starts discharge towards ground through R_B and Q_1 , with a time Const $R_B C$.

During the discharge the capacitor voltage is just less than $\frac{1}{3}V_{cc}$, the L_C is triggered i.e. $S=1$ and $R=0$ which turns $\bar{Q}=0$ and o/p = 1. The capacitor C is thus periodically charged and discharged between $\frac{2}{3}V_{cc}$ and $\frac{1}{3}V_{cc}$ respectively. The length of time that the o/p remains HIGH is the time for the capacitor charge from $\frac{1}{3}V_{cc}$ to $\frac{2}{3}V_{cc}$.