

## Comparators


A comparator which compares a signal voltage applied at one i/p of an op-amp with a known ref. voltage at the other i/p. It is basically an open loop op-amp with o/p  $\pm V_{sat}$  depending on which i/p is larger.

Basically two types of comparators are there

- ① Non-inverting comparator
- ② Inverting Comparator.

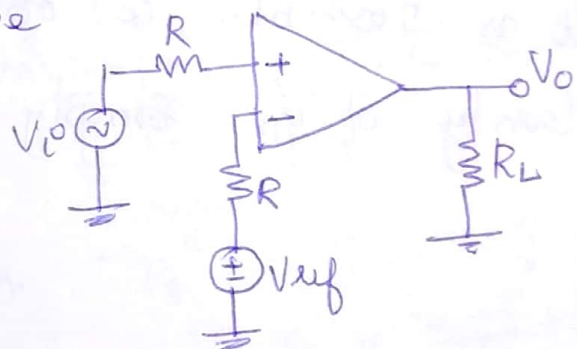
### Non-inverting comparator

A fixed ref. voltage is applied to -ve i/p and a time varying signal  $V_i$  is applied to +ve i/p.





$$\begin{aligned} \text{For } V_i < V_{ref} \quad V_o &= -V_{sat} \\ V_i > V_{ref} \quad V_o &= +V_{sat} \end{aligned}$$

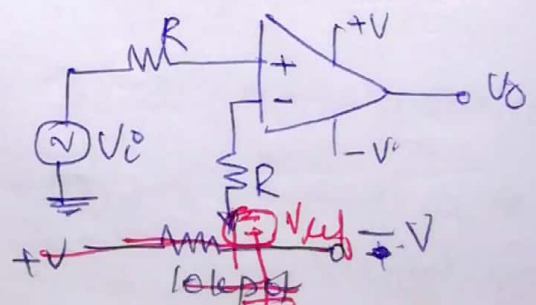In a practical ckt  $V_{ref}$  can be obtained by using a 10k pot




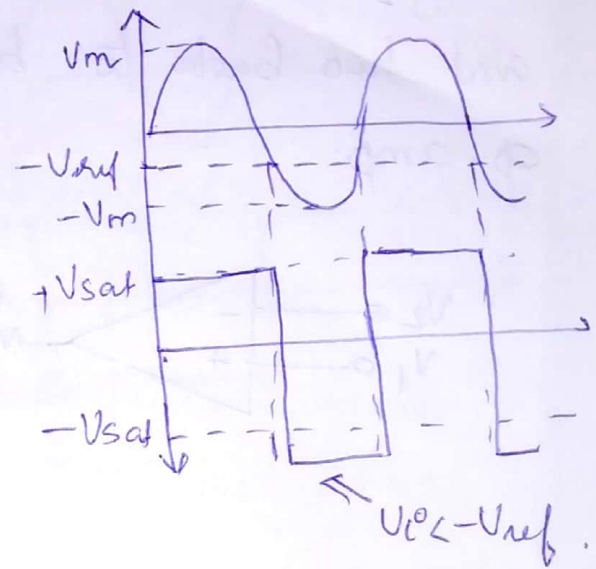
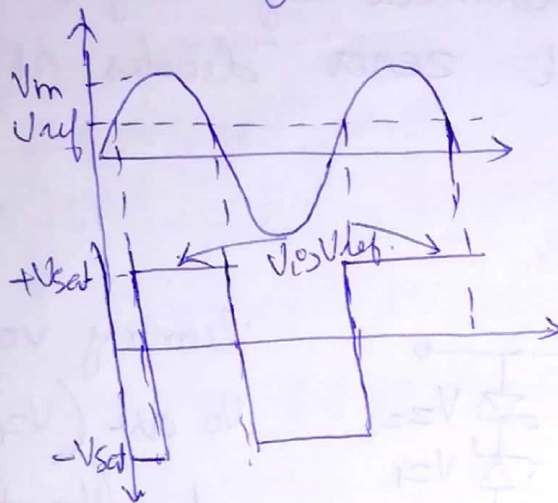
The op waveform for  $+ve V_{ref}$  and  $-ve V_{ref}$  are shown in fig



## Inverting Comparator


$V_{ref}$  is applied to the  $+ve$  terminal and  $V_i$  is the  $-ve$  terminal.

The op waveform is shown in fig

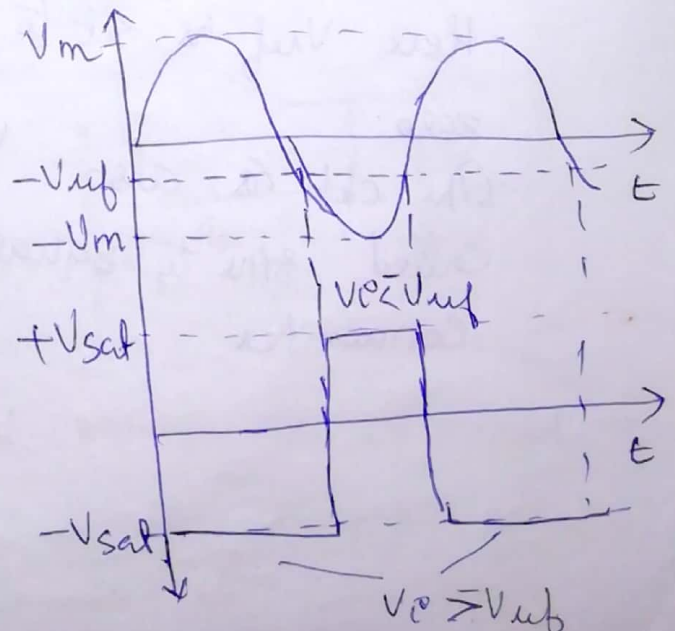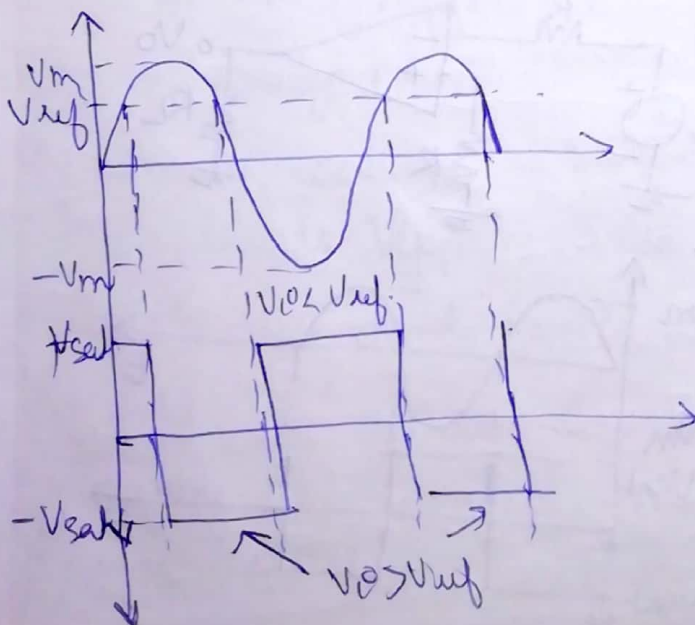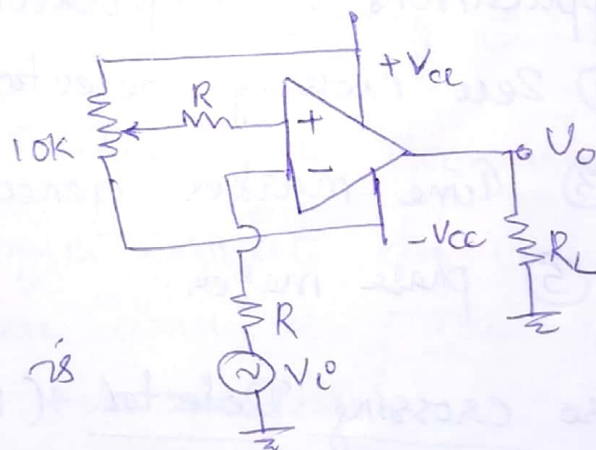



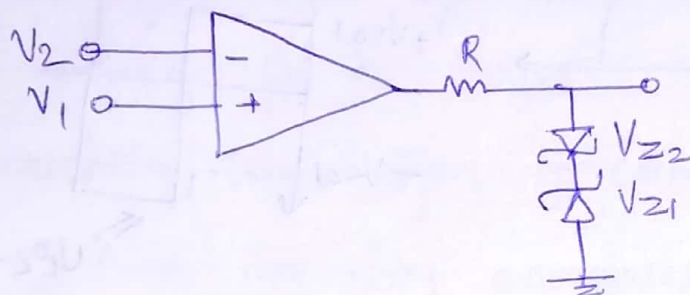op voltage levels independent of power supply voltages can also be obtained by using a resistor  $R$  and two back to back zener diodes at the op-amp.



limiting voltages of  $V_o$  are  $(V_{z1} + V_D)$  and  $-(V_{z2} + V_D)$  where  $V_D \approx 0.7V$ .


Applications of comparators are

- ① Zero crossing detector ② Window detector
- ③ Time marker generator ④ Time marker generator
- ⑤ phase meter.


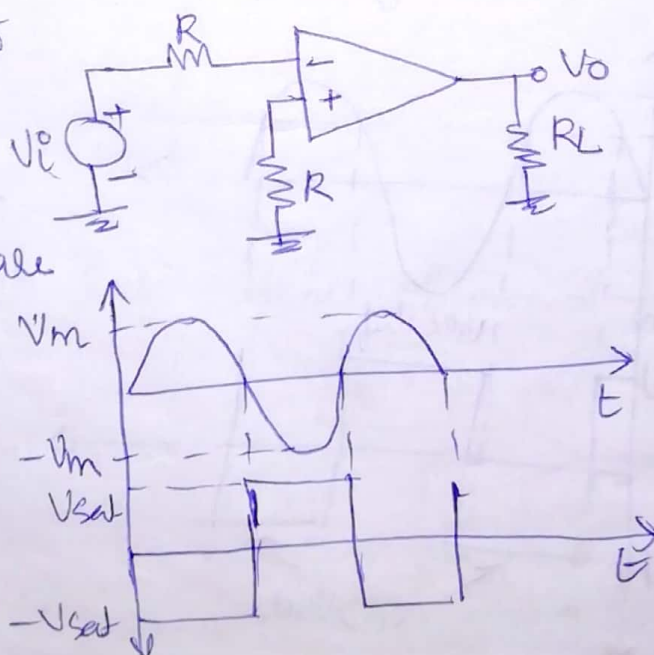
### Zero crossing Detector (Inverting)

Here  $V_{ref}$  is set to zero.

The ckt is also called sine to square converter.



## Non inverting Zero crossing detector

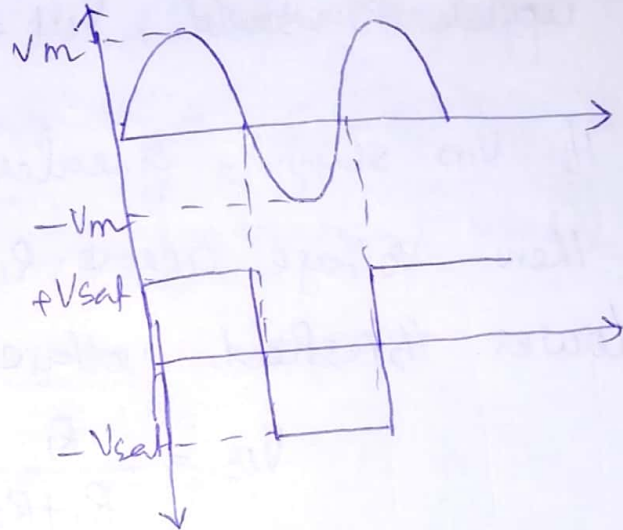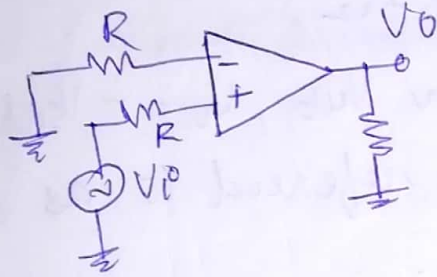

## Comparator characteristics

The important characteristics of comparator are

1. Speed of operation
2. Accuracy
3. Compatibility of o/p


## Schmitt Trigger (Regenerative Comparator)

Schmitt trigger converts an irregular shaped waveform to a square wave or pulse. It is an inv. comparator with +ve feedback.

The i/p  $V_{in}$  triggers the o/p  $V_o$  every time it exceeds certain voltage levels Upper

threshold  $V_{UT}$  and lower

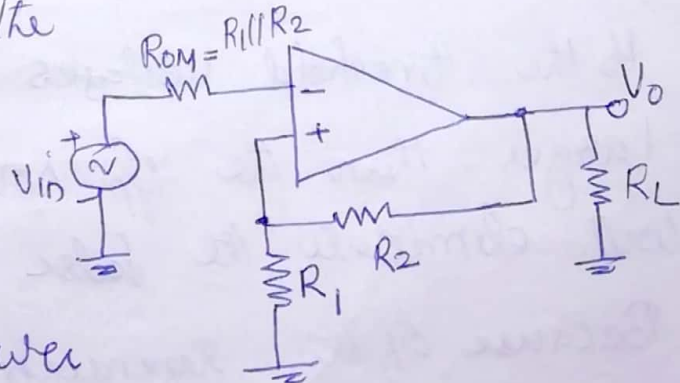threshold  $V_{LT}$ . These threshold voltages are obtained by using the voltage divider  $R_1 - R_2$  where voltage across  $R_1$  fed back to the +ve i/p.







when  $V_o = +V_{sat}$  voltage across  $R_1$  is called upper threshold,  $V_{ut} = \frac{R_1(+V_{sat})}{R_1+R_2}$ .

If  $V_{in}$  slightly greater than  $V_{ut}$ ,  $V_o = -V_{sat}$ .

then voltage across  $R_1$  is referred to as the lower threshold voltage  $V_{lt}$ .
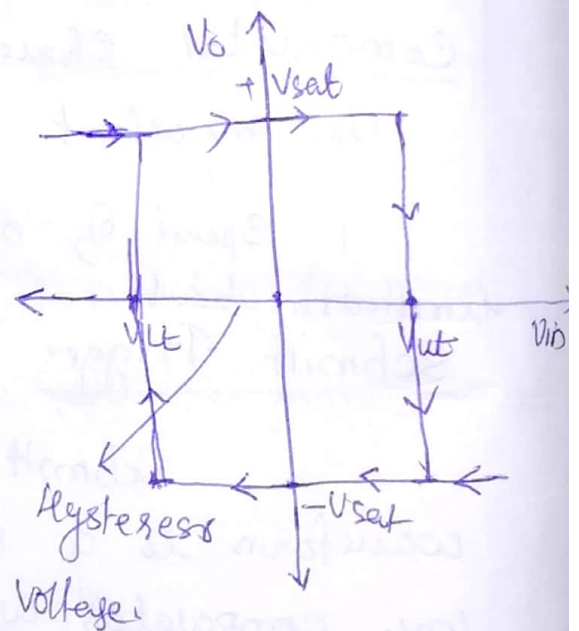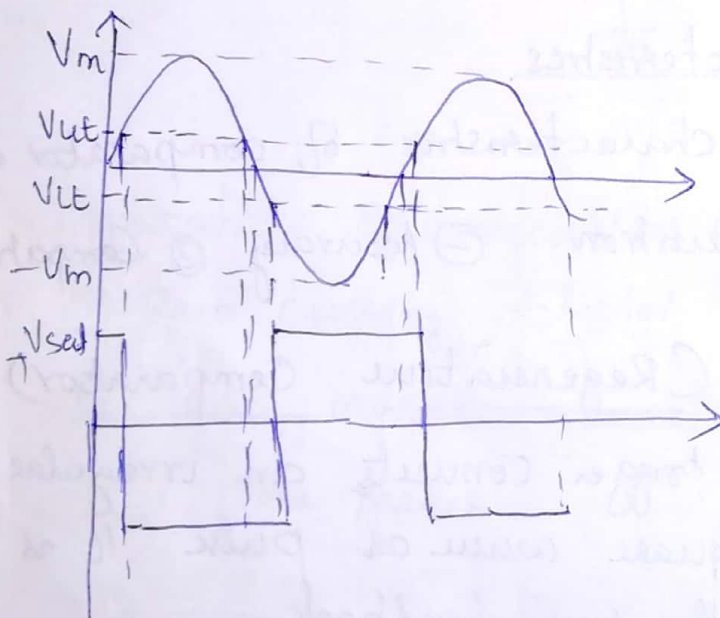
$$V_{lt} = \frac{R_1(-V_{sat})}{R_1+R_2}$$



If the threshold voltages  $V_{ut}$  and  $V_{lt}$  are made larger than the  $\uparrow \downarrow$  noise voltages, the  $\pm$ ve feedback will eliminate the false  $\uparrow \downarrow$  transitions.

Because of the regenerative action of  $\pm$ ve feedback  $V_o$  switch faster between  $+V_{sat}$  and  $-V_{sat}$ .

When  $\uparrow \downarrow$  triangular wave  $\uparrow \downarrow$  of schmitt trigger is square wave  
 " " Saw tooth " " pulse waveform

The comparator with +ve feedback said to exhibit hysteresis, a deadband condition

The hysteresis voltage  $V_{hy} = V_{ut} - V_{lt}$

$$= \frac{R_1}{R_1 + R_2} [ +V_{sat} - (-V_{sat}) ]$$

$$= \frac{R_1 (2V_{sat})}{R_1 + R_2}$$

---